

Lab4 Practice: LED Signal Control

You do NOT need to submit this practice

Description

- Control the LEDs by the BTNC (as the reset), BTNL, and BTNR buttons:
 - The output LED[15:0] will be reset to 16'b0. That is, all LEDs will be turned off upon the reset.
 - When the BTNL is pressed, turn on the leftmost darkened LED.
 - When all the LEDs are on, BTNL takes no effect.
 - When the BTNR is pressed, turn off the rightmost lightened LED.
 - When all the LEDs are off, BTNR takes no effect.
 - When either one of the BTNL or BTNR is pressed and held, the other button cannot trigger the operation.
 - Signals from the pushbuttons (except for the reset, i.e., rst) should be processed by the debounce circuit and one-pulse generator properly.

I/O signal specification

- **clk**: the clock signal with the frequency of 100MHz (connected to pin W5)
- **rst**: the asynchronous positive reset (connected to BTNC).
- **BTNL, BTNR**: the control pushbuttons.
- **LED[15:0]**: the signals to control LEDs (connected to **LD15 ~ LD0**).

HINT

1. You can use the following template for your design:

```
module lab4_practice (  
    input wire clk,  
    input wire rst,  
    input wire btnL,  
    input wire btnR,  
    output reg [15:0] LED  
);  
/* Note that output ports can be either reg or wire.  
 * It depends on how you design your module. */  
// add your design here  
endmodule
```

2. Demo video:

<https://drive.google.com/file/d/1Tjr5G7xteAoOB3FJAuNEuyfytGh2RKex/view?usp=sharing>